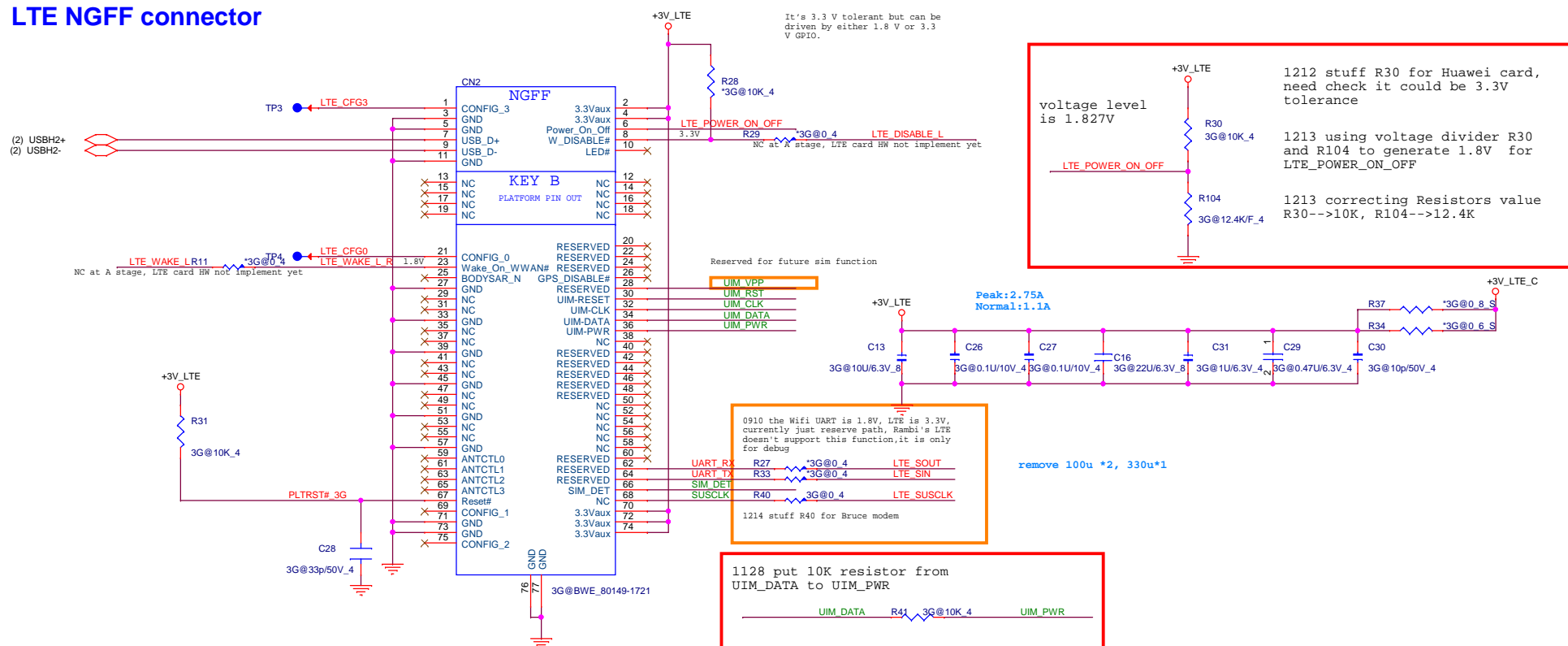


## LTE NGFF connector




## MultiMedia SIM (MNC)




20140120 change SIM connector to 9pin DFHS09FR212

<20090604(A1A)\_Qualcomm design guide>  
Place 0.1uF near connector's VCC pin

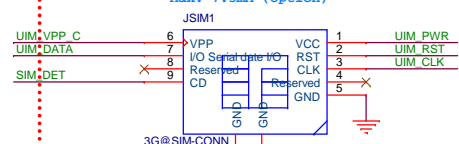
<Layout Notes> Keep USIM signals max length within 8000mils.  
Max: 7.5mA (Option)



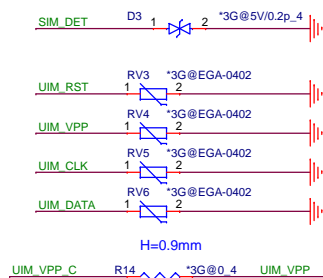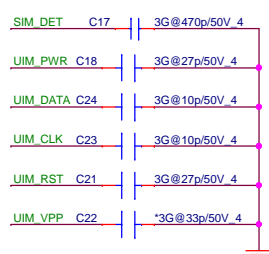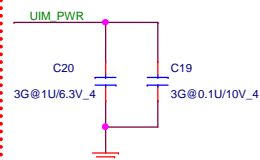DFHS09FR212 is used in proto1 and 1.5, due to shortage issue, change to second source DFHS07FR047 which is no pin 4 and 8



## IO Board Connector

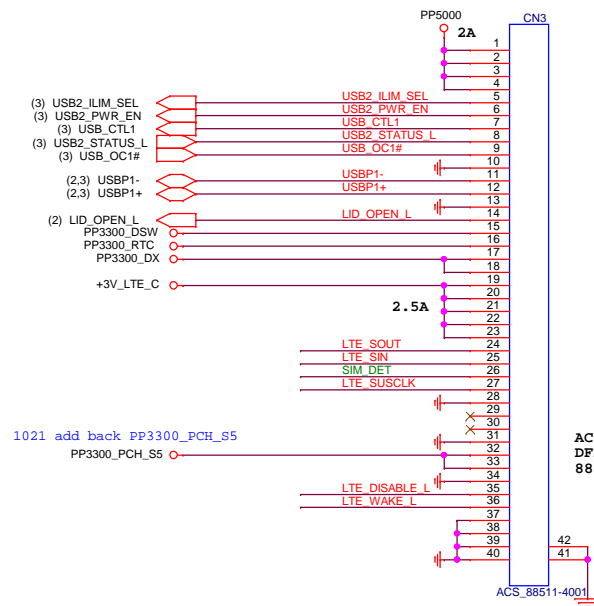

ACS  
DFFC40FR016  
88511-4001-40p-1



**Quanta Computer Inc.**

**PROJECT : 0C2A**


**LTE NGFF/SIM**

Date: Tuesday, March 25, 2014 Sheet 1 of 4

Date: Tuesday, March 25, 2014 Sheet 1 of 4


## USB HUB

1021 3G@HUB@ means HUB will be stuffed if 3G/LTE exists

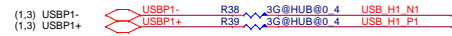

USB 2.0

LTE

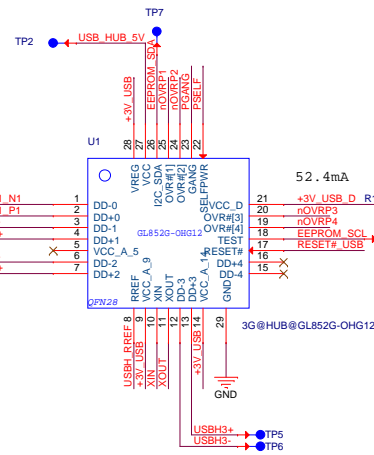



Follow vendor's suggestion(Close to pin 21)






1021 If USB2 external IO has wake up feature, HUE  
power need to be available in S5 +3V USB



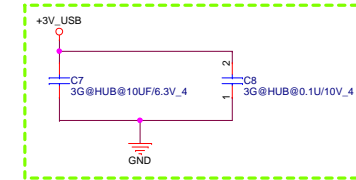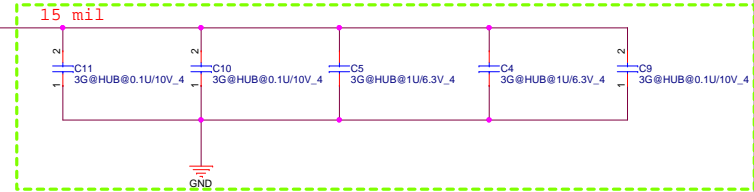
Follow vendor's suggestion(Close to GL850G-31)



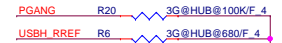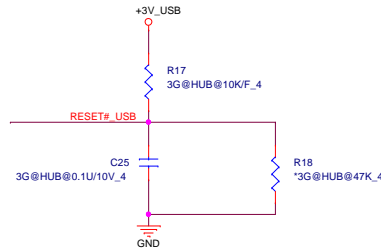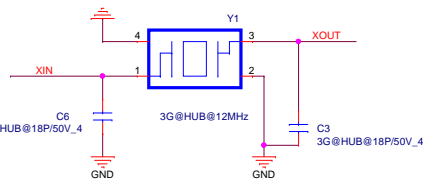
Follow vendor's suggestion(Close to pin 28)




## Lid Switch (HSR)

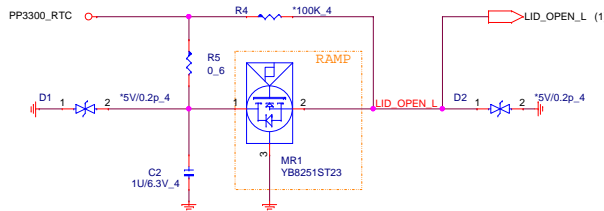


## Hole

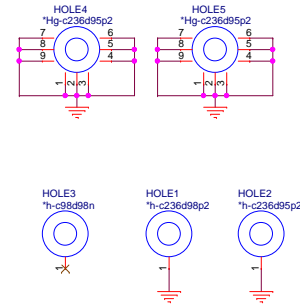

## USB 2.0

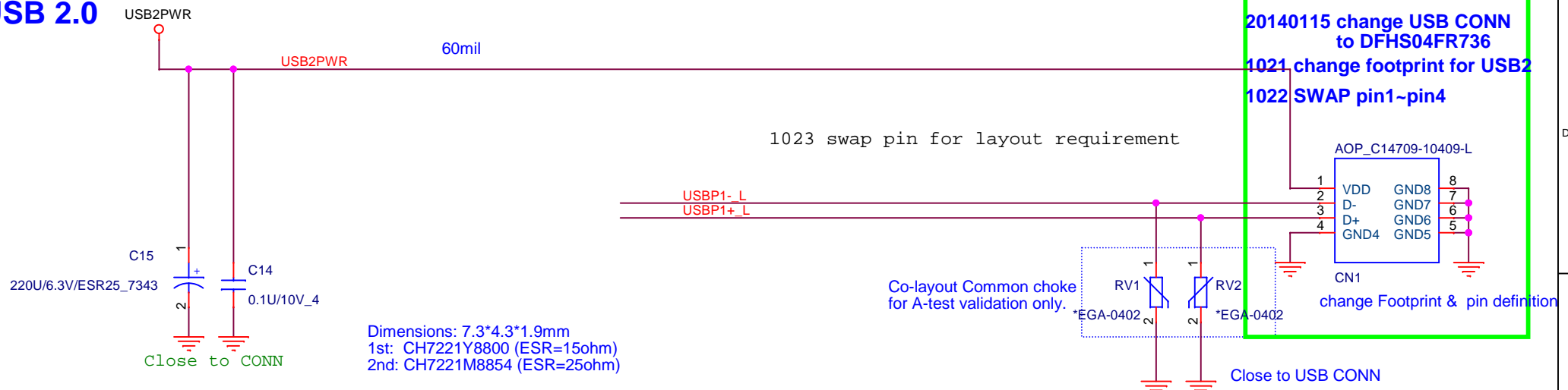

## USB Charger

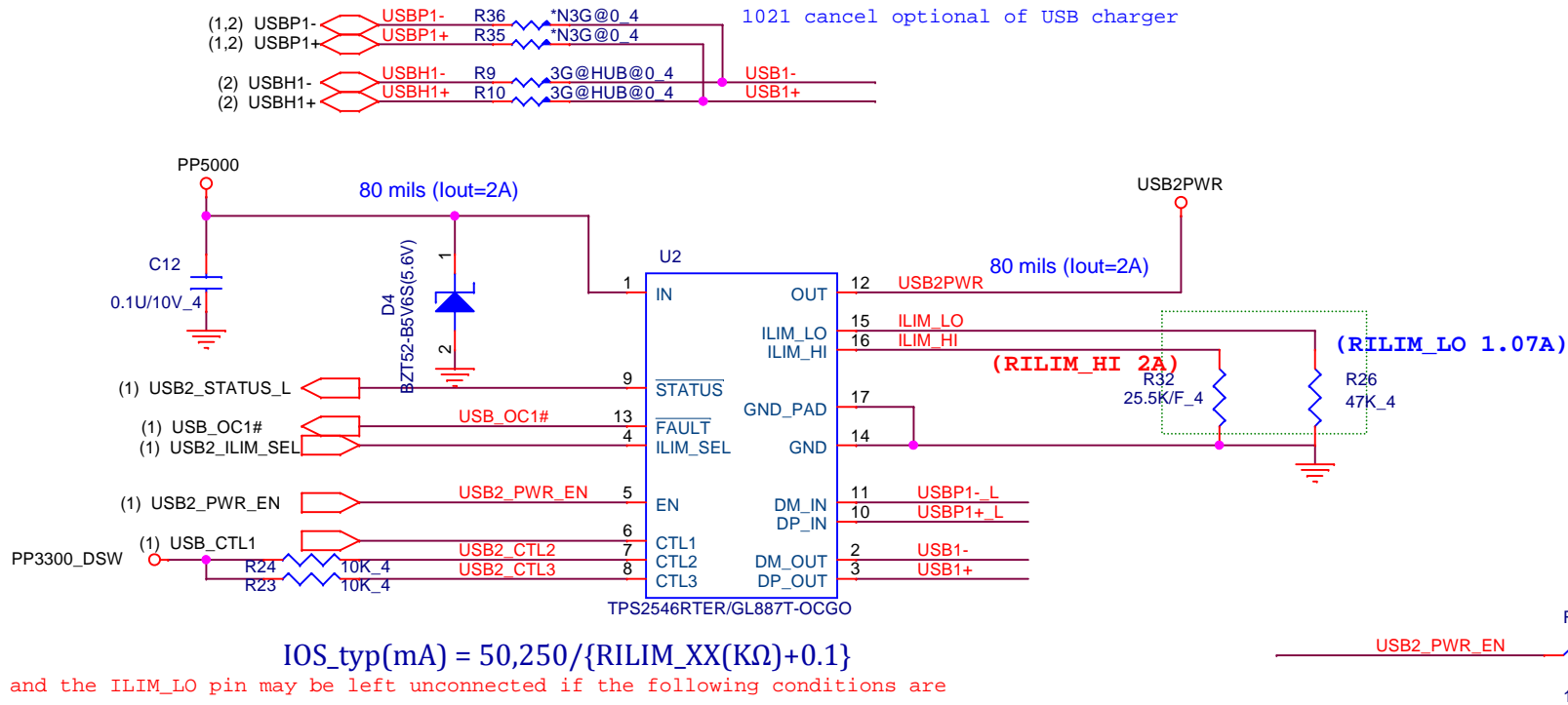

RILIM\_LO is optional and the ILIM\_LO pin may be left unconnected if the following conditions are met:


1. ILIM\_SEL is always set high
  2. Load Detection - Port Power Management is not used
  3. Mouse / Keyboard wake function is not used
- If conditions 1 and 2 are met but the mouse / keyboard wake function is also desired, it is recommended to use  
RILIM\_LO < 80.6 kΩ.  
The following equation programs the typical current limit:  
(1)  
RILIM\_XX corresponds to either RILIM\_HI or RILIM\_LO as appropriate.



**Quanta Computer Inc.**

**PROJECT : 0C2A**

Size	Document Number	Rev
	<b>USB 2.0/USB Charger</b>	2A
Date:	Tuesday, March 25, 2014	Sheet 3 of 4

Model	Version	CHANGE LIST
Chrome	1A	<p>1. update CN2 connecotr to DFFC24FS006 and footprint.  2. update CN22 connecotr to DFHS52FR107 and footprint.  3. update JSIM1 connecotr to DFHS09FR212 and footprint.  4. update CN17 connecotr to DFHD12MR046 and footprint.</p> <p>5. Net LTE_WAKE_L change connection from CN22 pin51 to pin1  6. Change net name +3v_mini2_VDD to +3v_VDD  7. Add 0 ohm in UIM_VPP</p> <p>8. Add Hole1 ~ Hole6  9. reverse CN2 pindefine  10.swap USB6+_R,USB6-_R</p> <p>11. Modify U1 pin20 net name.  12. Change Tp name and add TP  13. Change LTE to NGFF  14. Reserve 10KΩ pull up to LTE_POWER_ON_OFF  14. USB CN29 footprint &amp; pin define  14. change D35,D23 to 0402</p>
	2A	<p>1. Remove Card reader  2. Add USB HUB</p> <p>10/21  1. add back PP3300_PCH_S5  2. add back USB HUB power option (PP3300_PCH_S5)  3. 3G@HUB@ means HUB will be stuffed if 3G/LTE exists  4. cancel optional of USB charger  5. change footprint and PN for USB2,need check layout file again</p> <p>10/22  1. change USB connector pin definition for layout</p> <p>10/23  1. swap L27 pin for layout requirement</p> <p>10/24  1. Remove EEPROM U50.</p> <p>10/25  1. Reserve R40, add LTE_SUSCLK</p>
	3A	<p>11/28  1. put 10K resistor from UIM_DATA to UIM_PWR</p> <p>12/04  1. change SIM connector to 7pin DFHS07FR047</p> <p>12/12  1. stuff R30 for Huawei card, need check it could be 3.3V tolerance</p> <p>12/13  1. using voltage divider R30 and R104 to generate 1.8V for LTE_POWER_ON_OFF for Huawei card  2. correcting Resistors value R30--&gt;10K, R104--&gt;12.4K</p> <p>12/14  1. stuff R40 for Bruce modem</p>
<div> <div>  <div> <div>Quanta Computer Inc.</div> <div>PROJECT : 0C2A</div> </div> </div> <div> <div> <div>Size</div> <div>Document Number</div> </div> <div> <div>Change list</div> <div>Date: Tuesday, March 25, 2014</div> </div> </div> <div> <div>Rev</div> <div>2A</div> </div> <div> <div>Sheet</div> <div>4 of 4</div> </div> </div>		